

- Implement 8\*3 Encoder

  O The Encoder has 8 bits input, 3 bits output, and enable signal
- Write do file to compile & run simulation covering all cases.
- Bonus: In do files use loop to create simulation scenario [do files are TCL scripts]